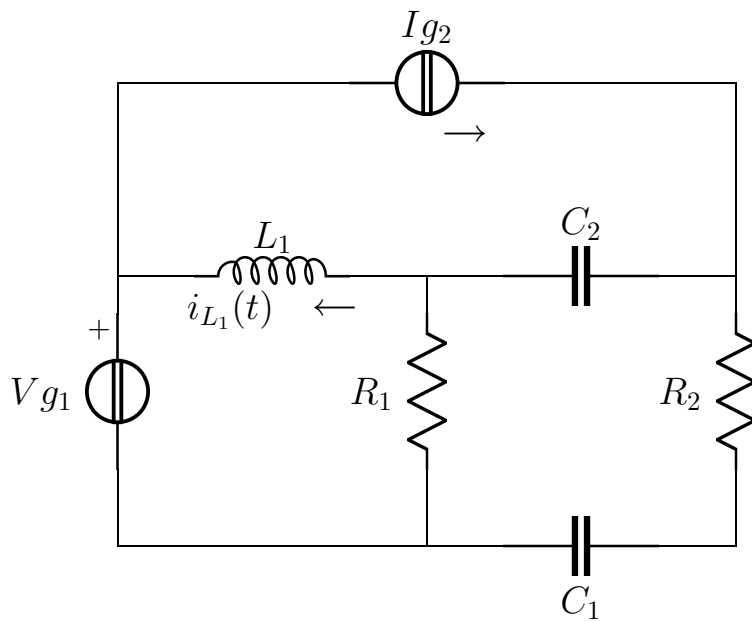


Esercizio C1 risolto

Risolvere il circuito in figura



$$\begin{aligned} v_{g1}(t) &= 10 \cos(2t + \arctan(\frac{3}{4})) \\ R_1 &= 2 \\ R_2 &= \frac{1}{2} \\ C_1 &= \frac{1}{2} \\ L_1 &= 2 \\ C_2 &= 1 \\ i_{g2}(t) &= \sqrt{2} \cos(2t + \frac{3\pi}{4}) \end{aligned}$$

Fasori

$$\mathbf{I}_{g2} = -1 + j$$

$$\mathbf{V}_{g1} = 8 + 6j$$


Semplificazioni serie/parallelo

$$Z_a = R_2 + \frac{1}{j\omega C_1} = \frac{1}{2} - j$$

$$Y_a = \frac{2}{5} + \frac{4}{5}j$$

Risoluzione dell'esercizio con il metodo delle maglie

Albero e coalbero:

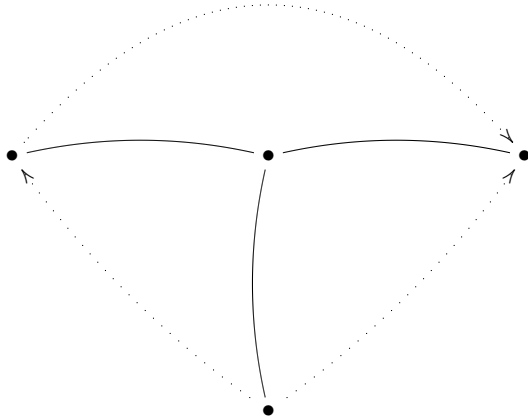

Sistema

$$\left\{ \begin{array}{rclcl} (R_1 + j\omega L_1)\mathbf{I}_1 & +R_1\mathbf{I}_2 & -j\omega L_1\mathbf{I}_3 & = & \mathbf{V}_{g1} \\ R_1\mathbf{I}_1 & +(R_1 + Z_a + \frac{1}{j\omega C_2})\mathbf{I}_2 & +\frac{1}{j\omega C_2}\mathbf{I}_3 & = & 0 \\ -j\omega L_1\mathbf{I}_1 & +\frac{1}{j\omega C_2}\mathbf{I}_2 & +(j\omega L_1 + \frac{1}{j\omega C_2})\mathbf{I}_3 & = & \mathbf{V}_{x2} \\ & & \mathbf{I}_3 & = & \mathbf{I}_{g2} \end{array} \right.$$

Sostituzione

$$\left\{ \begin{array}{rclcl} (2 + 4j)\mathbf{I}_1 & +2\mathbf{I}_2 & -4j\mathbf{I}_3 & = & 8 + 6j \\ 2\mathbf{I}_1 & +(\frac{5}{2} - \frac{3}{2}j)\mathbf{I}_2 & -\frac{1}{2}j\mathbf{I}_3 & = & 0 \\ -4j\mathbf{I}_1 & -\frac{1}{2}j\mathbf{I}_2 & +\frac{7}{2}j\mathbf{I}_3 & = & \mathbf{V}_{x2} \\ & & \mathbf{I}_3 & = & -1 + j \end{array} \right.$$

Soluzione

$$\left\{ \begin{array}{rcl} \mathbf{I}_1 & = & 1 - j \\ \mathbf{I}_2 & = & -1 \\ \mathbf{I}_3 & = & -1 + j \\ \mathbf{V}_{x2} & = & -\frac{15}{2} - 7j \end{array} \right.$$

Bilancio di potenza

Potenza complessa erogata dai generatori:

$$\begin{array}{ll} \mathbf{I}_{V_{g1}} = \mathbf{I}_1 = 1 - j & P_{c_{V_{g1}}} = \frac{1}{2} \mathbf{V}_{g1} \mathbf{I}_{V_{g1}}^* = 1 + 7j \\ \mathbf{V}_{I_{g2}} = \mathbf{V}_{x2} = -\frac{15}{2} - 7j & P_{c_{I_{g2}}} = \frac{1}{2} \mathbf{V}_{I_{g2}} \mathbf{I}_{g2}^* = \frac{1}{4} + \frac{29}{4}j \end{array}$$

$$P_{ctot} = \frac{5}{4} + \frac{57}{4}j$$

Potenza attiva assorbita dai resistori:

$$\begin{aligned}\mathbf{I}_{\mathbf{R}_1} &= -\mathbf{I}_1 - \mathbf{I}_2 = j & P_{a_{R_1}} &= \frac{1}{2}R_1|\mathbf{I}_{\mathbf{R}_1}|^2 = 1 \\ \mathbf{I}_{\mathbf{R}_2} &= \mathbf{I}_2 = -1 & P_{a_{R_2}} &= \frac{1}{2}R_2|\mathbf{I}_{\mathbf{R}_2}|^2 = \frac{1}{4} \\ P_{a_{tot}} &= \frac{5}{4} = \Re\{P_{c_{tot}}\}\end{aligned}$$

Potenza reattiva assorbita dai condensatori e induttori:

$$\begin{aligned}\mathbf{I}_{\mathbf{L}_1} &= -\mathbf{I}_1 + \mathbf{I}_3 = -2 + 2j & Q_{L_1} &= \frac{1}{2}\omega L_1|\mathbf{I}_{\mathbf{L}_1}|^2 = 16 \\ \mathbf{V}_{\mathbf{C}_2} &= (-\mathbf{I}_2 - \mathbf{I}_3)\frac{1}{j\omega C_2} = -\frac{1}{2} - j & Q_{C_2} &= -\frac{1}{2}\omega C_2|\mathbf{V}_{\mathbf{C}_2}|^2 = -\frac{5}{4} \\ \mathbf{V}_{\mathbf{C}_1} &= \frac{\mathbf{I}_2}{j\omega C_1} = j & Q_{C_1} &= -\frac{1}{2}\omega C_1|\mathbf{V}_{\mathbf{C}_1}|^2 = -\frac{1}{2} \\ Q_{tot} &= \frac{57}{4} = \Im\{P_{c_{tot}}\}\end{aligned}$$

Calcolo tensioni e correnti

$$\begin{aligned}\mathbf{I}_{\mathbf{L}_1} &= -\mathbf{I}_1 + \mathbf{I}_3 = -2 + 2j \\ i_{L_1}(t) &= 2\sqrt{2}\cos\left(2t + \frac{3\pi}{4}\right)\end{aligned}$$

Soluzioni:

$$\begin{aligned}V_{g_1} &= 8 + 6j; & I_{g_1} &= 1 - j; & P_{c_{V_{g_1}}} &= 1 + 7j \\ V_{R_1} &= -2j; & I_{R_1} &= j; & P_{a_{R_1}} &= 1 \\ V_{R_2} + V_{C_1} &= \frac{1}{2} - j; & I_{R_2} &= I_{C_1} = -1; & P_{a_{R_2}} &= \frac{1}{4} \\ Q_{C_1} &= -\frac{1}{2} \\ V_{L_1} &= -8 - 8j; & I_{L_1} &= 2 - 2j; & Q_{L_1} &= 16 \\ V_{C_2} &= \frac{1}{2} + j; & I_{C_2} &= 2 - j; & Q_{C_2} &= -\frac{5}{4} \\ V_{g_2} &= -\frac{15}{2} - 7j; & I_{g_2} &= -1 + j; & P_{c_{I_{g_2}}} &= \frac{1}{4} + \frac{29}{4}j\end{aligned}$$