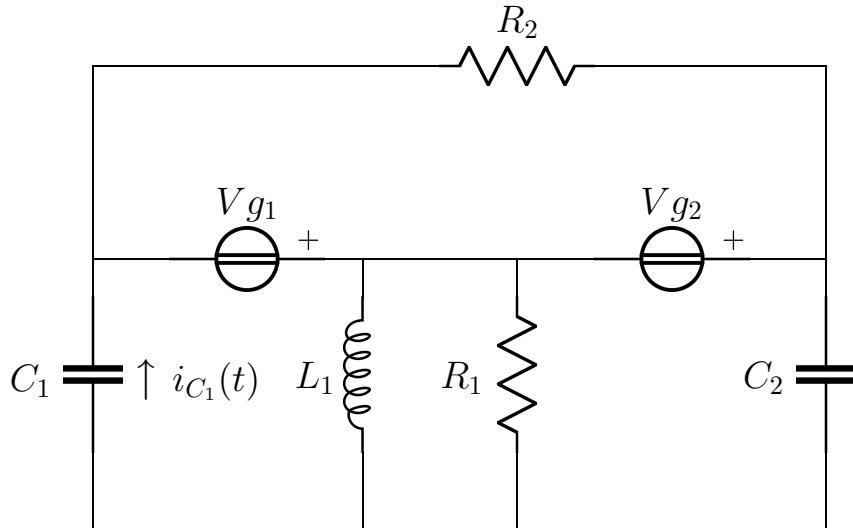


Esercizio C2 risolto

Risolvere il circuito in figura



$$\begin{aligned}
 C_1 &= 2 \\
 R_1 &= 1 \\
 L_1 &= \frac{1}{16} \\
 C_2 &= \frac{1}{2} \\
 v_{g_1}(t) &= \cos(2t) \\
 v_{g_2}(t) &= \sqrt{2} \cos\left(2t - \frac{\pi}{4}\right) \\
 R_2 &= \frac{1}{2}
 \end{aligned}$$

Fasori

$$\mathbf{V}_{g_2} = 1 - j$$

$$\mathbf{V}_{g_1} = 1$$

Semplificazioni serie/parallelo

$$Y_a = \frac{1}{R_1} + \frac{1}{j\omega L_1} = 1 - 8j$$

$$Z_a = \frac{1}{65} + \frac{8}{65}j$$

Risoluzione dell'esercizio con il metodo dei nodi

Sistema

$$\left\{
 \begin{array}{lcl}
 (j\omega C_1 + \frac{1}{R_2})\mathbf{E}_1 & -\frac{1}{R_2}\mathbf{E}_2 & -j\omega C_1\mathbf{E}_3 = -\mathbf{I}_{x_1} \\
 -\frac{1}{R_2}\mathbf{E}_1 & +(j\omega C_2 + \frac{1}{R_2})\mathbf{E}_2 & -j\omega C_2\mathbf{E}_3 = \mathbf{I}_{x_2} \\
 -j\omega C_1\mathbf{E}_1 & -j\omega C_2\mathbf{E}_2 & +(j\omega C_1 + Y_a + j\omega C_2)\mathbf{E}_3 = 0 \\
 -\mathbf{E}_1 & \mathbf{E}_2 & = \mathbf{V}_{g_1} \\
 & & = \mathbf{V}_{g_2}
 \end{array}
 \right.$$

Sostituzione

$$\left\{ \begin{array}{lcl} (2+4j)\mathbf{E}_1 & -2\mathbf{E}_2 & -4j\mathbf{E}_3 = -\mathbf{I}_{x_1} \\ -2\mathbf{E}_1 & +(2+j)\mathbf{E}_2 & -j\mathbf{E}_3 = \mathbf{I}_{x_2} \\ -4j\mathbf{E}_1 & -j\mathbf{E}_2 & +(1-3j)\mathbf{E}_3 = 0 \\ -\mathbf{E}_1 & & = 1 \\ & \mathbf{E}_2 & = 1-j \end{array} \right.$$

Soluzione

$$\left\{ \begin{array}{lcl} \mathbf{E}_1 & = & -1 \\ \mathbf{E}_2 & = & 1-j \\ \mathbf{E}_3 & = & 1 \\ \mathbf{I}_{x_1} & = & 4+6j \\ \mathbf{I}_{x_2} & = & 5-2j \end{array} \right.$$

Bilancio di potenza

Potenza complessa erogata dai generatori:

$$\begin{aligned} \mathbf{I}_{V_{g1}} = \mathbf{I}_{x_2} &= 4+6j & P_{c_{Vg1}} &= \frac{1}{2}\mathbf{V}_{g1}\mathbf{I}_{V_{g1}}^* = 2-3j \\ \mathbf{I}_{V_{g2}} = \mathbf{I}_{x_2} &= 5-2j & P_{c_{Vg2}} &= \frac{1}{2}\mathbf{V}_{g2}\mathbf{I}_{V_{g2}}^* = \frac{7}{2}-\frac{3}{2}j \\ P_{c_{tot}} &= \frac{11}{2}-\frac{9}{2}j \end{aligned}$$

Potenza attiva assorbita dai resistori:

$$\begin{aligned} \mathbf{I}_{R_1} &= \frac{-\mathbf{E}_3}{R_1} = -1 & P_{a_{R_1}} &= \frac{1}{2}R_1|\mathbf{I}_{R_1}|^2 = \frac{1}{2} \\ \mathbf{I}_{R_2} &= \frac{\mathbf{E}_2-\mathbf{E}_1}{R_2} = 4-2j & P_{a_{R_2}} &= \frac{1}{2}R_2|\mathbf{I}_{R_2}|^2 = 5 \\ P_{a_{tot}} &= \frac{11}{2} = \Re\{P_{c_{tot}}\} \end{aligned}$$

Potenza reattiva assorbita dai condensatori e induttori:

$$\begin{aligned} \mathbf{V}_{C_1} = \mathbf{E}_3 - \mathbf{E}_1 &= 2 & Q_{C_1} &= -\frac{1}{2}\omega C_1 |\mathbf{V}_{C_1}|^2 = -8 \\ \mathbf{V}_{C_2} = \mathbf{E}_2 - \mathbf{E}_3 &= -j & Q_{C_2} &= -\frac{1}{2}\omega C_2 |\mathbf{V}_{C_2}|^2 = -\frac{1}{2} \\ \mathbf{I}_{L_1} = \frac{-\mathbf{E}_3}{j\omega L_1} &= 8j & Q_{L_1} &= \frac{1}{2}\omega L_1 |\mathbf{I}_{L_1}|^2 = 4 \\ Q_{tot} &= -\frac{9}{2} = \Im\{P_{c_{tot}}\} \end{aligned}$$

Calcolo tensioni e correnti

$$\mathbf{I}_{C_1} = (\mathbf{E}_3 - \mathbf{E}_1)j\omega C_1 = 8j$$

$$i_{C_1}(t) = 8 \cos\left(2t + \frac{\pi}{2}\right)$$

Soluzioni:

$$\begin{aligned}
 V_{C_1} &= -2; & I_{C_1} &= 8j; & Q_{C_1} &= -8 \\
 V_{R_1} = V_{L_1} &= -1; & I_{R_1} + I_{L_1} &= 1 - 8j; & Pa_{R_1} &= \frac{1}{2} \\
 Q_{L_1} &= 4 \\
 V_{C_2} &= -j; & I_{C_2} &= -1; & Q_{C_2} &= -\frac{1}{2} \\
 V_{g_1} &= 1; & I_{g_1} &= 4 + 6j; & P_{cV_{g1}} &= 2 - 3j \\
 V_{g_2} &= 1 - j; & I_{g_2} &= 5 - 2j; & P_{cV_{g2}} &= \frac{7}{2} - \frac{3}{2}j \\
 V_{R_2} &= 2 - j; & I_{R_2} &= -4 + 2j; & Pa_{R_2} &= 5
 \end{aligned}$$