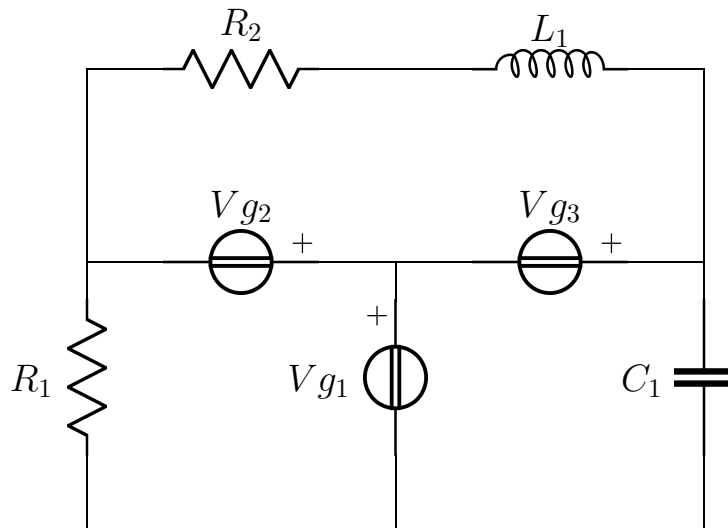


Esercizio d1 risolto 2

Risolvere il circuito in figura



$$\begin{aligned} R_1 &= 1 \\ v_{g_1}(t) &= \cos(t + \pi) \\ C_1 &= 1 \\ v_{g_2}(t) &= \cos\left(t + \frac{\pi}{2}\right) \\ v_{g_3}(t) &= 2 \cos(t) \\ R_2 &= 2 \\ L_1 &= 1 \end{aligned}$$

Fasori


$$\begin{aligned} \mathbf{V}_{g_3} &= 2 \\ \mathbf{V}_{g_2} &= j \\ \mathbf{V}_{g_1} &= -1 \end{aligned}$$

Semplificazioni serie/parallelo

$$\begin{aligned} Z_a &= R_2 + j\omega L_1 = 2 + j \\ Y_a &= \frac{2}{5} - \frac{1}{5}j \end{aligned}$$

Risoluzione dell'esercizio con il metodo delle maglie

Albero e coalbero:

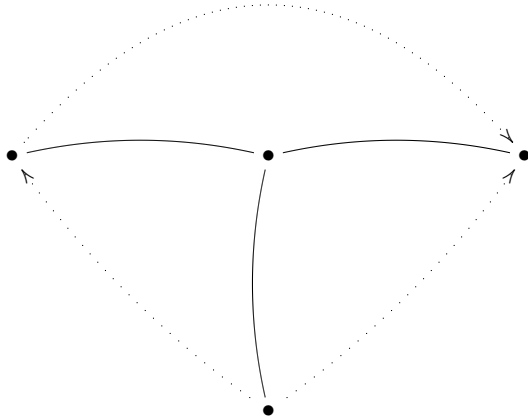

Sistema

$$\begin{cases} R_1 \mathbf{I}_1 & = -\mathbf{V}_{g1} + \mathbf{V}_{g2} \\ \frac{1}{j\omega C_1} \mathbf{I}_2 & = -\mathbf{V}_{g1} - \mathbf{V}_{g3} \\ Z_a \mathbf{I}_3 & = -\mathbf{V}_{g2} - \mathbf{V}_{g3} \end{cases}$$

Sostituzione

$$\begin{cases} \mathbf{I}_1 & = 1 + j \\ -j\mathbf{I}_2 & = -1 \\ (2 + j)\mathbf{I}_3 & = -2 - j \end{cases}$$

Soluzione

$$\begin{cases} \mathbf{I}_1 & = 1 + j \\ \mathbf{I}_2 & = -j \\ \mathbf{I}_3 & = -1 \end{cases}$$

Bilancio di potenza

Potenza complessa erogata dai generatori:

$$\begin{aligned} \mathbf{I}_{V_{g1}} &= -\mathbf{I}_1 - \mathbf{I}_2 = -1 & P_{cV_{g1}} &= \frac{1}{2} \mathbf{V}_{g1} \mathbf{I}_{V_{g1}}^* = \frac{1}{2} \\ \mathbf{I}_{V_{g2}} &= \mathbf{I}_1 - \mathbf{I}_3 = 2 + j & P_{cV_{g2}} &= \frac{1}{2} \mathbf{V}_{g2} \mathbf{I}_{V_{g2}}^* = \frac{1}{2} + j \\ \mathbf{I}_{V_{g3}} &= -\mathbf{I}_2 - \mathbf{I}_3 = 1 + j & P_{cV_{g3}} &= \frac{1}{2} \mathbf{V}_{g3} \mathbf{I}_{V_{g3}}^* = 1 - j \end{aligned}$$

$$P_{c_{tot}} = 2$$

Potenza attiva assorbita dai resistori:

$$\begin{aligned} \mathbf{I}_{R1} &= \mathbf{I}_1 = 1 + j & P_{aR1} &= \frac{1}{2} R_1 |\mathbf{I}_{R1}|^2 = 1 \\ \mathbf{I}_{R2} &= \mathbf{I}_3 = -1 & P_{aR2} &= \frac{1}{2} R_2 |\mathbf{I}_{R2}|^2 = 1 \end{aligned}$$

$$P_{a_{tot}} = 2 = \Re\{P_{c_{tot}}\}$$

Potenza reattiva assorbita dai condensatori e induttori:

$$\begin{aligned} \mathbf{V}_{C_1} &= \mathbf{I}_2 \frac{1}{j\omega C_1} = -1 & Q_{C_1} &= -\frac{1}{2}\omega C_1 |\mathbf{V}_{C_1}|^2 = -\frac{1}{2} \\ \mathbf{I}_{L_1} &= \mathbf{I}_3 = -1 & Q_{L_1} &= \frac{1}{2}\omega L_1 |\mathbf{I}_{L_1}|^2 = \frac{1}{2} \end{aligned}$$

$$Q_{tot} = 0 = \Im\{P_{c_{tot}}\}$$

Soluzioni:

$$\begin{array}{lll} V_{R_1} = -1 - j; & I_{R_1} = 1 + j; & Pa_{R_1} = 1 \\ V_{g_1} = -1; & I_{g_1} = -1; & Pc_{V_{g_1}} = \frac{1}{2} \\ V_{C_1} = 1; & I_{C_1} = -j; & Q_{C_1} = -\frac{1}{2} \\ V_{g_2} = j; & I_{g_2} = 2 + j; & Pc_{V_{g_2}} = \frac{1}{2} + j \\ V_{g_3} = 2; & I_{g_3} = 1 + j; & Pc_{V_{g_3}} = 1 - j \\ V_{R_2} + V_{L_1} = 2 + j; & I_{R_2} = I_{L_1} = -1; & Pa_{R_2} = 1 \\ Q_{L_1} = \frac{1}{2} \end{array}$$