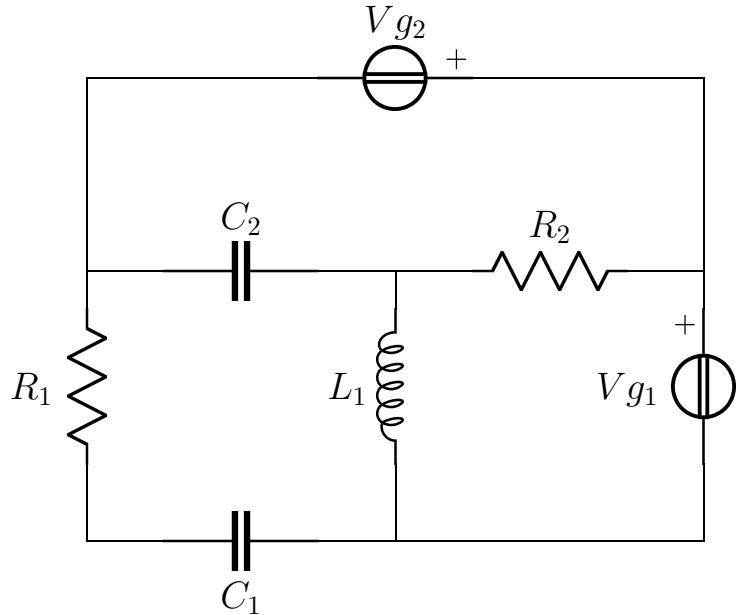


Esercizio c1 risolto 2

Risolvere il circuito in figura



$R_1 = \frac{3}{2}$
$C_1 = \frac{1}{11}$
$L_1 = 2$
$v_{g_1}(t) = 6\sqrt{2} \cos(2t + \frac{3\pi}{4})$
$C_2 = \frac{1}{2}$
$R_2 = 2$
$v_{g_2}(t) = \sqrt{5} \cos(2t + \arctan(2))$

Fasori

$$\mathbf{V}_{g_2} = 1 + 2j$$

$$\mathbf{V}_{g_1} = -6 + 6j$$


Semplificazioni serie/parallelo

$$Z_a = R_1 + \frac{1}{j\omega C_1} = \frac{3}{2} - \frac{11}{2}j$$

$$Y_a = \frac{3}{65} + \frac{11}{65}j$$

Risoluzione dell'esercizio con il metodo delle maglie

Albero e coalbero:

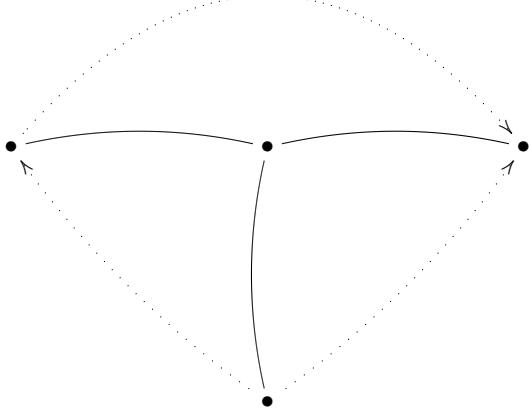

Sistema

$$\left\{ \begin{array}{lcl} (Z_a + j\omega L_1 + \frac{1}{j\omega C_2})\mathbf{I}_1 & +j\omega L_1 \mathbf{I}_2 & -\frac{1}{j\omega C_2} \mathbf{I}_3 = 0 \\ j\omega L_1 \mathbf{I}_1 & +(j\omega L_1 + R_2) \mathbf{I}_2 & +R_2 \mathbf{I}_3 = \mathbf{V}_{g_1} \\ -\frac{1}{j\omega C_2} \mathbf{I}_1 & +R_2 \mathbf{I}_2 & +(\frac{1}{j\omega C_2} + R_2) \mathbf{I}_3 = \mathbf{V}_{g_2} \end{array} \right.$$

Sostituzione

$$\left\{ \begin{array}{lcl} (\frac{3}{2} - \frac{5}{2}j)\mathbf{I}_1 & +4j \mathbf{I}_2 & +j \mathbf{I}_3 = 0 \\ 4j \mathbf{I}_1 & +(2 + 4j) \mathbf{I}_2 & +2 \mathbf{I}_3 = -6 + 6j \\ j \mathbf{I}_1 & +2 \mathbf{I}_2 & +(2 - j) \mathbf{I}_3 = 1 + 2j \end{array} \right.$$

Soluzione

$$\left\{ \begin{array}{lcl} \mathbf{I}_1 & = & 1 + j \\ \mathbf{I}_2 & = & j \\ \mathbf{I}_3 & = & 1 \end{array} \right.$$

Bilancio di potenza

Potenza complessa erogata dai generatori:

$$\begin{aligned} \mathbf{I} \mathbf{V}_{g1} &= \mathbf{I}_2 = j & P_{c_{Vg1}} &= \frac{1}{2} \mathbf{V}_{g1} \mathbf{I}_{Vg1}^* = 3 + 3j \\ \mathbf{I} \mathbf{V}_{g2} &= \mathbf{I}_3 = 1 & P_{c_{Vg2}} &= \frac{1}{2} \mathbf{V}_{g2} \mathbf{I}_{Vg2}^* = \frac{1}{2} + j \end{aligned}$$

$$P_{c_{tot}} = \frac{7}{2} + 4j$$

Potenza attiva assorbita dai resistori:

$$\begin{aligned} \mathbf{I}_{R1} &= \mathbf{I}_1 = 1 + j & P_{a_{R1}} &= \frac{1}{2} R_1 |\mathbf{I}_{R1}|^2 = \frac{3}{2} \\ \mathbf{I}_{R2} &= -\mathbf{I}_2 - \mathbf{I}_3 = -1 - j & P_{a_{R2}} &= \frac{1}{2} R_2 |\mathbf{I}_{R2}|^2 = 2 \end{aligned}$$

$$P_{a_{tot}} = \frac{7}{2} = \Re e\{P_{c_{tot}}\}$$

Potenza reattiva assorbita dai condensatori e induttori:

$$\begin{aligned}\mathbf{I}_{\mathbf{L}_1} &= -\mathbf{I}_1 - \mathbf{I}_2 = -1 - 2j & Q_{L_1} &= \frac{1}{2}\omega L_1 |\mathbf{I}_{\mathbf{L}_1}|^2 = 10 \\ \mathbf{V}_{\mathbf{C}_2} &= (\mathbf{I}_1 - \mathbf{I}_3) \frac{1}{j\omega C_2} = 1 & Q_{C_2} &= -\frac{1}{2}\omega C_2 |\mathbf{V}_{\mathbf{C}_2}|^2 = -\frac{1}{2} \\ \mathbf{V}_{\mathbf{C}_1} &= \frac{\mathbf{I}_1}{j\omega C_1} = \frac{11}{2} - \frac{11}{2}j & Q_{C_1} &= -\frac{1}{2}\omega C_1 |\mathbf{V}_{\mathbf{C}_1}|^2 = -\frac{11}{2}\end{aligned}$$

$$Q_{tot} = 4 = \Im m\{P_{c_{tot}}\}$$

Soluzioni:

$$\begin{aligned}V_{R_1} + V_{C_1} &= -7 + 4j; & I_{R_1} = I_{C_1} &= 1 + j; & Pa_{R_1} &= \frac{3}{2} \\ Q_{C_1} &= -\frac{11}{2} \\ V_{L_1} &= -8 + 4j; & I_{L_1} &= -1 - 2j; & Q_{L_1} &= 10 \\ V_{g_1} &= -6 + 6j; & I_{g_1} &= j; & P_{c_{V_{g_1}}} &= 3 + 3j \\ V_{C_2} &= -1; & I_{C_2} &= j; & Q_{C_2} &= -\frac{1}{2} \\ V_{R_2} &= 2 + 2j; & I_{R_2} &= -1 - j; & Pa_{R_2} &= 2 \\ V_{g_2} &= 1 + 2j; & I_{g_2} &= 1; & P_{c_{V_{g_2}}} &= \frac{1}{2} + j\end{aligned}$$