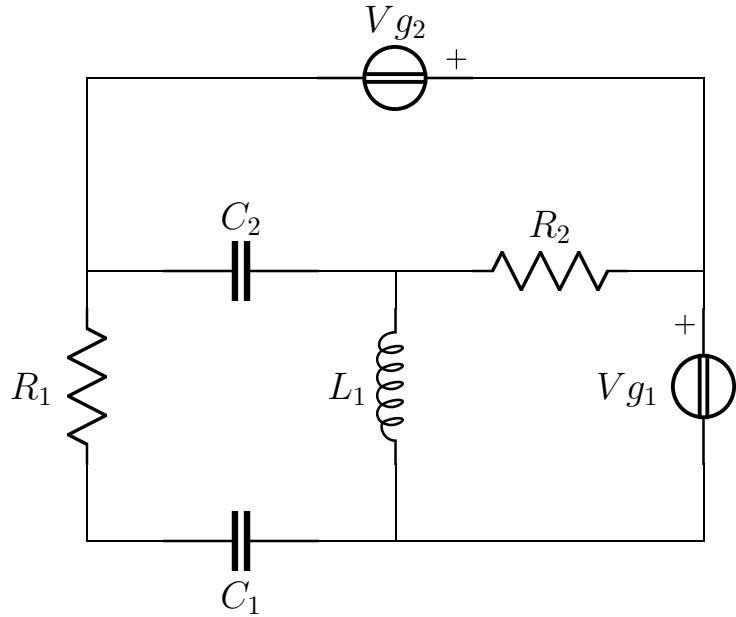


# Esercizio c1 risolto 1

Risolvere il circuito in figura



$R_1 = \frac{3}{2}$
$C_1 = \frac{1}{11}$
$L_1 = 2$
$v_{g_1}(t) = 6\sqrt{2} \cos(2t + \frac{3\pi}{4})$
$C_2 = \frac{1}{2}$
$R_2 = 2$
$v_{g_2}(t) = \sqrt{5} \cos(2t + \arctan(2))$

## Fasori

$$\mathbf{V}_{g_2} = 1 + 2j$$

$$\mathbf{V}_{g_1} = -6 + 6j$$

## Semplificazioni serie/parallelo

$$Z_a = R_1 + \frac{1}{j\omega C_1} = \frac{3}{2} - \frac{11}{2}j$$

$$Y_a = \frac{3}{65} + \frac{11}{65}j$$

## Risoluzione dell'esercizio con il metodo dei nodi

Sistema

$$\left\{ \begin{array}{lcl} (Y_a + j\omega C_2)\mathbf{E}_1 & -j\omega C_2\mathbf{E}_2 & -Y_a\mathbf{E}_3 = -\mathbf{I}_{x_2} \\ -j\omega C_2\mathbf{E}_1 + (\frac{1}{j\omega L_1} + j\omega C_2 + \frac{1}{R_2})\mathbf{E}_2 & -\frac{1}{j\omega L_1}\mathbf{E}_3 = 0 \\ -Y_a\mathbf{E}_1 & -\frac{1}{j\omega L_1}\mathbf{E}_2 + (Y_a + \frac{1}{j\omega L_1})\mathbf{E}_3 = -\mathbf{I}_{x_1} \\ -\mathbf{E}_1 & -\mathbf{E}_3 = \mathbf{V}_{g_1} & = \mathbf{V}_{g_2} \end{array} \right.$$

Sostituzione

$$\left\{ \begin{array}{l} (\frac{3}{65} + \frac{76}{65}j)\mathbf{E}_1 - j\mathbf{E}_2 + (-\frac{3}{65} - \frac{11}{65}j)\mathbf{E}_3 = -\mathbf{I}_{x_2} \\ -j\mathbf{E}_1 + (\frac{1}{2} + \frac{3}{4}j)\mathbf{E}_2 + \frac{1}{4}j\mathbf{E}_3 = 0 \\ (-\frac{3}{65} - \frac{11}{65}j)\mathbf{E}_1 + \frac{1}{4}j\mathbf{E}_2 + (\frac{3}{65} - \frac{8}{99}j)\mathbf{E}_3 = -\mathbf{I}_{x_1} \\ -\mathbf{E}_3 = -6 + 6j \\ -\mathbf{E}_1 = 1 + 2j \end{array} \right.$$

Soluzione

$$\left\{ \begin{array}{l} \mathbf{E}_1 = -1 - 2j \\ \mathbf{E}_2 = -2 - 2j \\ \mathbf{E}_3 = 6 - 6j \\ \mathbf{I}_{x_1} = j \\ \mathbf{I}_{x_2} = 1 \end{array} \right.$$

### Bilancio di potenza

Potenza complessa erogata dai generatori:

$$\mathbf{I}_{V_{g1}} = \mathbf{I}_{x_g 1} = j \quad P_{c_{V_{g1}}} = \frac{1}{2}\mathbf{V}_{g1}\mathbf{I}_{V_{g1}}^* = 3 + 3j$$

$$\mathbf{I}_{V_{g2}} = \mathbf{I}_{x_g 1} = 1 \quad P_{c_{V_{g2}}} = \frac{1}{2}\mathbf{V}_{g2}\mathbf{I}_{V_{g2}}^* = \frac{1}{2} + j$$

$$P_{c_{tot}} = \frac{7}{2} + 4j$$

Potenza attiva assorbita dai resistori:

$$\mathbf{I}_{R_1} = \frac{\mathbf{E}_1 - \mathbf{E}_3}{Z_a} = -1 - 1j \quad P_{a_{R_1}} = \frac{1}{2}R_1|\mathbf{I}_{R_1}|^2 = \frac{3}{2}$$

$$\mathbf{I}_{R_2} = \frac{-\mathbf{E}_2}{R_2} = 1 + j \quad P_{a_{R_2}} = \frac{1}{2}R_2|\mathbf{I}_{R_2}|^2 = 2$$

$$P_{a_{tot}} = \frac{7}{2} = \Re\{P_{c_{tot}}\}$$

Potenza reattiva assorbita dai condensatori e induttori:

$$\mathbf{I}_{L_1} = \frac{\mathbf{E}_2 - \mathbf{E}_3}{j\omega L_1} = 1 + 2j \quad Q_{L_1} = \frac{1}{2}\omega L_1|\mathbf{I}_{L_1}|^2 = 10$$

$$\mathbf{V}_{C_2} = \mathbf{E}_2 - \mathbf{E}_1 = -1 \quad Q_{C_2} = -\frac{1}{2}\omega C_2|\mathbf{V}_{C_2}|^2 = -\frac{1}{2}$$

$$\mathbf{V}_{C_1} = \frac{(\mathbf{E}_1 - \mathbf{E}_3)Y_a}{j\omega C_1} = -\frac{11}{2} + \frac{11}{2}j \quad Q_{C_1} = -\frac{1}{2}\omega C_1|\mathbf{V}_{C_1}|^2 = -\frac{11}{2}$$

$$Q_{tot} = 4 = \Im\{P_{c_{tot}}\}$$

**Soluzioni:**

$$\begin{aligned} V_{R_1} + V_{C_1} &= -7 + 4j; & I_{R_1} = I_{C_1} &= 1 + j; & Pa_{R_1} &= \frac{3}{2} \\ Q_{C_1} &= -\frac{11}{2} & I_{L_1} &= -1 - 2j; & Q_{L_1} &= 10 \\ V_{L_1} &= -8 + 4j; & I_{g_1} &= j; & P_{cV_{g1}} &= 3 + 3j \\ V_{g_1} &= -6 + 6j; & I_{C_2} &= j; & Q_{C_2} &= -\frac{1}{2} \\ V_{C_2} &= -1; & I_{R_2} &= -1 - j; & Pa_{R_2} &= 2 \\ V_{R_2} &= 2 + 2j; & I_{g_2} &= 1; & P_{cV_{g2}} &= \frac{1}{2} + j \\ V_{g_2} &= 1 + 2j; & & & & \end{aligned}$$