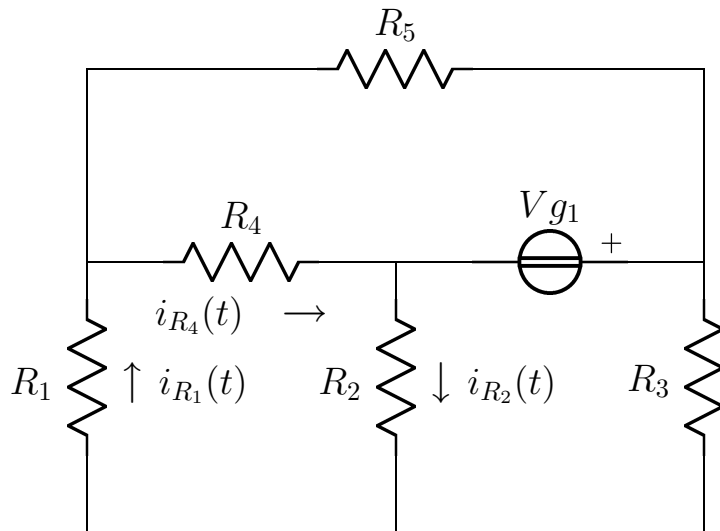


# Esercizio resistori


Risolvere il circuito in figura



$$\begin{aligned} R_1 &= 1 \\ R_2 &= \frac{1}{5} \\ R_3 &= \frac{1}{2} \\ R_4 &= 2 \\ V_{g1} &= 3 \\ R_5 &= \frac{1}{2} \end{aligned}$$

Risoluzione dell'esercizio con il metodo delle maglie

Albero e coalbero:

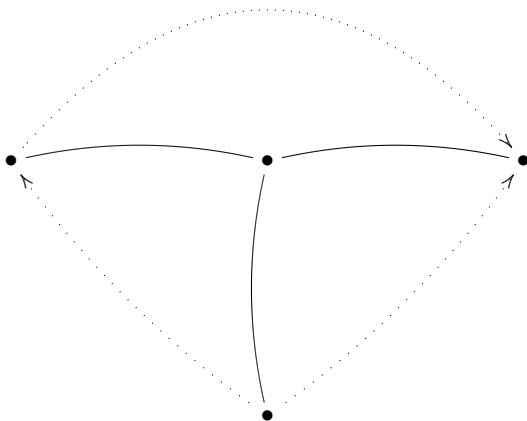

Sistema

$$\left\{ \begin{array}{rcl} (R_1 + R_2 + R_4)\mathbf{I}_1 & + R_2\mathbf{I}_2 & - R_4\mathbf{I}_3 = 0 \\ R_2\mathbf{I}_1 & + (R_2 + R_3)\mathbf{I}_2 & = -\mathbf{V}_{g1} \\ -R_4\mathbf{I}_1 & & + (R_4 + R_5)\mathbf{I}_3 = -\mathbf{V}_{g1} \end{array} \right.$$

Sostituzione

$$\left\{ \begin{array}{rcl} \frac{16}{5}\mathbf{I}_1 & + \frac{1}{5}\mathbf{I}_2 & - 2\mathbf{I}_3 = 0 \\ \frac{1}{5}\mathbf{I}_1 & + \frac{7}{10}\mathbf{I}_2 & = -3 \\ -2\mathbf{I}_1 & & + \frac{5}{2}\mathbf{I}_3 = -3 \end{array} \right.$$

Soluzione

$$\left\{ \begin{array}{rcl} \mathbf{I}_1 & = & -1 \\ \mathbf{I}_2 & = & -4 \\ \mathbf{I}_3 & = & -2 \end{array} \right.$$

### Bilancio di potenza

Potenza complessa erogata dai generatori:

$$\mathbf{I}_{V_{g1}} = -\mathbf{I}_2 - \mathbf{I}_3 = 6 \quad P_{c_{V_{g1}}} = \frac{1}{2} \mathbf{V}_{g1} \mathbf{I}_{V_{g1}}^* = 9$$

$$P_{c_{tot}} = 9$$

Potenza attiva assorbita dai resistori:

$$\begin{array}{ll} \mathbf{I}_{R_1} = \mathbf{I}_1 = -1 & P_{a_{R_1}} = \frac{1}{2} R_1 |\mathbf{I}_{R_1}|^2 = \frac{1}{2} \\ \mathbf{I}_{R_2} = \mathbf{I}_1 + \mathbf{I}_2 = -5 & P_{a_{R_2}} = \frac{1}{2} R_2 |\mathbf{I}_{R_2}|^2 = \frac{5}{2} \\ \mathbf{I}_{R_3} = \mathbf{I}_2 = -4 & P_{a_{R_3}} = \frac{1}{2} R_3 |\mathbf{I}_{R_3}|^2 = 4 \\ \mathbf{I}_{R_4} = \mathbf{I}_1 - \mathbf{I}_3 = 1 & P_{a_{R_4}} = \frac{1}{2} R_4 |\mathbf{I}_{R_4}|^2 = 1 \\ \mathbf{I}_{R_5} = \mathbf{I}_3 = -2 & P_{a_{R_5}} = \frac{1}{2} R_5 |\mathbf{I}_{R_5}|^2 = 1 \end{array}$$

$$P_{a_{tot}} = 9 = \Re\{P_{c_{tot}}\}$$

Potenza reattiva assorbita dai condensatori e induttori:

$$Q_{tot} = 0 = \Im\{P_{c_{tot}}\}$$

### Calcolo tensioni e correnti

$$\mathbf{I}_{\mathbf{R}_1} = \mathbf{I}_1 = -1$$

$$i_{R_1}(t) = \cos(t + \pi)$$

$$\mathbf{I}_{\mathbf{R}_2} = \mathbf{I}_1 + \mathbf{I}_2 = -5$$

$$i_{R_2}(t) = 5 \cos(t + \pi)$$

$$\mathbf{I}_{\mathbf{R}_4} = \mathbf{I}_1 - \mathbf{I}_3 = 1$$

$$i_{R_4}(t) = \cos(t)$$

### Soluzioni:

$$V_{R_1} = 1; \quad I_{R_1} = -1; \quad Pa_{R_1} = \frac{1}{2}$$

$$V_{R_2} = -1; \quad I_{R_2} = 5; \quad Pa_{R_2} = \frac{5}{2}$$

$$V_{R_3} = 2; \quad I_{R_3} = -4; \quad Pa_{R_3} = 4$$

$$V_{R_4} = -2; \quad I_{R_4} = 1; \quad Pa_{R_4} = 1$$

$$V_{g_1} = 3; \quad I_{g_1} = 6; \quad Pc_{V_{g_1}} = 9$$

$$V_{R_5} = 1; \quad I_{R_5} = -2; \quad Pa_{R_5} = 1$$