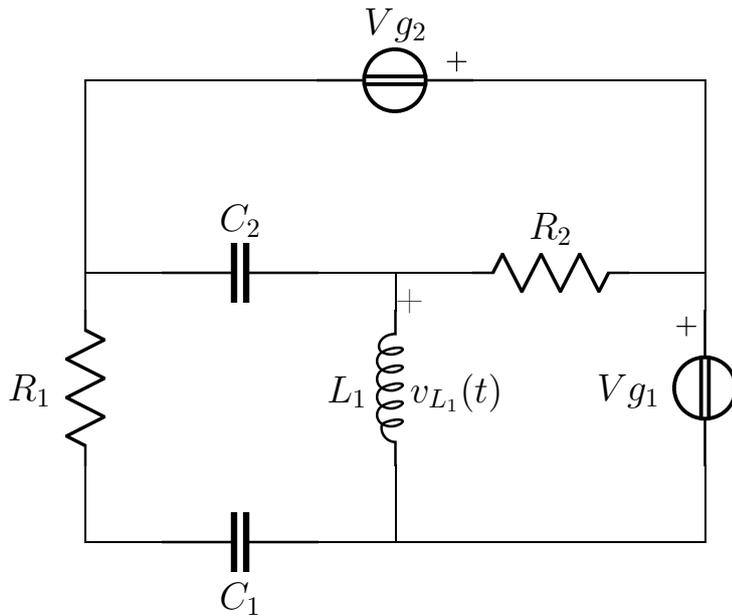


Esercizio salerno3

Risolvere il circuito in figura



$R_1 = \frac{3}{2}$
$C_1 = \frac{1}{11}$
$L_1 = 2$
$\mathbf{V}_{g1} = -6 + 6j$
$C_2 = \frac{1}{2}$
$R_2 = 2$
$\mathbf{V}_{g2} = 1 + 2j$
$\omega = 2$

Semplificazioni serie/parallelo

$$Z_a = R_1 + \frac{1}{j\omega C_1} = \frac{3}{2} - \frac{11}{2}j$$

$$Y_a = \frac{3}{65} + \frac{11}{65}j$$

Risoluzione dell'esercizio con il metodo dei nodi

Sistema

$$\left\{ \begin{array}{l} (Y_a + j\omega C_2)\mathbf{E}_1 - j\omega C_2\mathbf{E}_2 - Y_a\mathbf{E}_3 = -\mathbf{I}_{x2} \\ -j\omega C_2\mathbf{E}_1 + (\frac{1}{j\omega L_1} + j\omega C_2 + \frac{1}{R_2})\mathbf{E}_2 - \frac{1}{j\omega L_1}\mathbf{E}_3 = 0 \\ -Y_a\mathbf{E}_1 - \frac{1}{j\omega L_1}\mathbf{E}_2 + (Y_a + \frac{1}{j\omega L_1})\mathbf{E}_3 = -\mathbf{I}_{x1} \\ -\mathbf{E}_3 = \mathbf{V}_{g1} \\ -\mathbf{E}_1 = \mathbf{V}_{g2} \end{array} \right.$$

Sostituzione

$$\left\{ \begin{array}{l} \left(\frac{3}{65} + \frac{76}{65}j \right) \mathbf{E}_1 - j \mathbf{E}_2 + \left(-\frac{3}{65} - \frac{11}{65}j \right) \mathbf{E}_3 = -\mathbf{I}_{x_2} \\ -j \mathbf{E}_1 + \left(\frac{1}{2} + \frac{3}{4}j \right) \mathbf{E}_2 + \frac{1}{4}j \mathbf{E}_3 = 0 \\ \left(-\frac{3}{65} - \frac{11}{65}j \right) \mathbf{E}_1 + \frac{1}{4}j \mathbf{E}_2 + \left(\frac{3}{65} - \frac{8}{99}j \right) \mathbf{E}_3 = -\mathbf{I}_{x_1} \\ -\mathbf{E}_3 = -6 + 6j \\ -\mathbf{E}_1 = 1 + 2j \end{array} \right.$$

Soluzione

$$\left\{ \begin{array}{l} \mathbf{E}_1 = -1 - 2j \\ \mathbf{E}_2 = -2 - 2j \\ \mathbf{E}_3 = 6 - 6j \\ \mathbf{I}_{x_1} = j \\ \mathbf{I}_{x_2} = 1 \end{array} \right.$$

Bilancio di potenza

Potenza complessa erogata dai generatori:

$$\begin{aligned} \mathbf{I}_{V_{g1}} = \mathbf{I}_{x_{g1}} = j \quad P_{cV_{g1}} = \frac{1}{2} \mathbf{V}_{g1} \mathbf{I}_{V_{g1}}^* = 3 + 3j \\ \mathbf{I}_{V_{g2}} = \mathbf{I}_{x_{g1}} = 1 \quad P_{cV_{g2}} = \frac{1}{2} \mathbf{V}_{g2} \mathbf{I}_{V_{g2}}^* = \frac{1}{2} + j \end{aligned}$$

$$P_{ctot} = \frac{7}{2} + 4j$$

Potenza attiva assorbita dai resistori:

$$\begin{aligned} \mathbf{I}_{R_1} = \frac{\mathbf{E}_1 - \mathbf{E}_3}{Z_a} = -1 - 1j \quad P_{aR_1} = \frac{1}{2} R_1 |\mathbf{I}_{R_1}|^2 = \frac{3}{2} \\ \mathbf{I}_{R_2} = \frac{-\mathbf{E}_2}{R_2} = 1 + j \quad P_{aR_2} = \frac{1}{2} R_2 |\mathbf{I}_{R_2}|^2 = 2 \end{aligned}$$

$$P_{atot} = \frac{7}{2} = \Re\{P_{ctot}\}$$

Potenza reattiva assorbita dai condensatori e induttori:

$$\begin{aligned} \mathbf{I}_{L_1} = \frac{\mathbf{E}_2 - \mathbf{E}_3}{j\omega L_1} = 1 + 2j \quad Q_{L_1} = \frac{1}{2} \omega L_1 |\mathbf{I}_{L_1}|^2 = 10 \\ \mathbf{V}_{C_2} = \mathbf{E}_2 - \mathbf{E}_1 = -1 \quad Q_{C_2} = -\frac{1}{2} \omega C_2 |\mathbf{V}_{C_2}|^2 = -\frac{1}{2} \\ \mathbf{V}_{C_1} = \frac{(\mathbf{E}_1 - \mathbf{E}_3) Y_a}{j\omega C_1} = -\frac{11}{2} + \frac{11}{2}j \quad Q_{C_1} = -\frac{1}{2} \omega C_1 |\mathbf{V}_{C_1}|^2 = -\frac{11}{2} \end{aligned}$$

$$Q_{tot} = 4 = \Im\{P_{ctot}\}$$

Calcolo tensioni e correnti

$$\mathbf{V}_{L_1} = \mathbf{E}_2 - \mathbf{E}_3 = -8 + 4j$$

$$v_{L_1}(t) = 4\sqrt{5} \cos(2t - \arctan(\frac{1}{2}) + \pi)$$

Soluzioni:

$$\begin{array}{lll} V_{R_1} + V_{C_1} = -7 + 4j; & I_{R_1} = I_{C_1} = 1 + j; & Pa_{R_1} = \frac{3}{2} \\ Q_{C_1} = -\frac{11}{2} & & \\ V_{L_1} = -8 + 4j; & I_{L_1} = -1 - 2j; & Q_{L_1} = 10 \\ V_{g_1} = -6 + 6j; & I_{g_1} = j; & Pc_{V_{g_1}} = 3 + 3j \\ V_{C_2} = -1; & I_{C_2} = j; & Q_{C_2} = -\frac{1}{2} \\ V_{R_2} = 2 + 2j; & I_{R_2} = -1 - j; & Pa_{R_2} = 2 \\ V_{g_2} = 1 + 2j; & I_{g_2} = 1; & Pc_{V_{g_2}} = \frac{1}{2} + j \end{array}$$