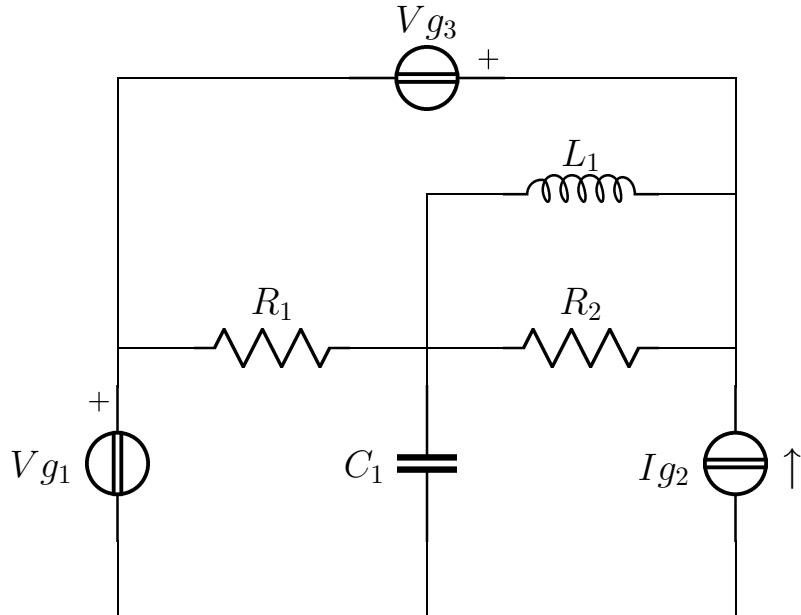


Esercizio ggcesame2015 – 02 – 24B3Nodi_rif1

Risolvere il circuito in figura



$\mathbf{V}_{g_1} = -2$
$C_1 = 1$
$\mathbf{I}_{g_2} = -1$
$R_1 = 2$
$R_2 = 1$
$L_1 = 1$
$\mathbf{V}_{g_3} = 1 + 2j$
$\omega = 1$

Semplificazioni serie/parallelo

$$Y_a = \frac{1}{R_2} + \frac{1}{j\omega L_1} = 1 - j$$

$$Z_a = \frac{1}{2} + \frac{1}{2}j$$

Risoluzione dell'esercizio con il metodo dei nodi

Sistema

$$\left\{ \begin{array}{lcl} (j\omega C_1 + \frac{1}{R_1} + Y_a)\mathbf{E}_1 & -Y_a\mathbf{E}_2 & -j\omega C_1\mathbf{E}_3 \\ -Y_a\mathbf{E}_1 & +Y_a\mathbf{E}_2 & = \mathbf{I}_{g_2} + \mathbf{I}_{x_3} \\ -j\omega C_1\mathbf{E}_1 & +j\omega C_1\mathbf{E}_3 & = -\mathbf{I}_{g_2} - \mathbf{I}_{x_1} \\ \mathbf{E}_2 & -\mathbf{E}_3 & = \mathbf{V}_{g_1} \\ & & = \mathbf{V}_{g_3} \end{array} \right.$$

Sostituzione

$$\left\{ \begin{array}{lcl} \frac{3}{2}\mathbf{E}_1 + (-1+j)\mathbf{E}_2 - j\mathbf{E}_3 & = & 0 \\ (-1+j)\mathbf{E}_1 + (1-j)\mathbf{E}_2 & = & -1 + \mathbf{I}_{x_3} \\ -j\mathbf{E}_1 & & +j\mathbf{E}_3 = 1 - \mathbf{I}_{x_1} \\ & & -\mathbf{E}_3 = -2 \\ & & \mathbf{E}_2 = 1 + 2j \end{array} \right.$$

Soluzione

$$\left\{ \begin{array}{lcl} \mathbf{E}_1 & = & 2 + 2j \\ \mathbf{E}_2 & = & 1 + 2j \\ \mathbf{E}_3 & = & 2 \\ \mathbf{I}_{x_1} & = & -1 \\ \mathbf{I}_{x_3} & = & j \end{array} \right.$$

Bilancio di potenza

Potenza complessa erogata dai generatori:

$$\begin{aligned} \mathbf{I}_{V_{g1}} &= \mathbf{I}_{x_2} = -1 & P_{c_{V_{g1}}} &= \frac{1}{2}\mathbf{V}_{g1}\mathbf{I}_{V_{g1}}^* = 1 \\ \mathbf{V}_{I_{g2}} &= \mathbf{E}_2 - \mathbf{E}_3 = -1 + 2j & P_{c_{I_{g2}}} &= \frac{1}{2}\mathbf{V}_{I_{g2}}\mathbf{I}_{g2}^* = \frac{1}{2} - j \\ \mathbf{I}_{V_{g3}} &= \mathbf{I}_{x_2} = j & P_{c_{V_{g3}}} &= \frac{1}{2}\mathbf{V}_{g3}\mathbf{I}_{V_{g3}}^* = 1 - \frac{1}{2}j \\ P_{c_{tot}} &= \frac{5}{2} - \frac{3}{2}j \end{aligned}$$

Potenza attiva assorbita dai resistori:

$$\begin{aligned} \mathbf{I}_{R_1} &= \frac{\mathbf{E}_1}{R_1} = 1 + j & P_{a_{R_1}} &= \frac{1}{2}R_1|\mathbf{I}_{R_1}|^2 = 2 \\ \mathbf{I}_{R_2} &= \frac{\mathbf{E}_2 - \mathbf{E}_1}{R_2} = -1 & P_{a_{R_2}} &= \frac{1}{2}R_2|\mathbf{I}_{R_2}|^2 = \frac{1}{2} \\ P_{a_{tot}} &= \frac{5}{2} = \Re\{P_{c_{tot}}\} \end{aligned}$$

Potenza reattiva assorbita dai condensatori e induttori:

$$\begin{aligned} \mathbf{V}_{C_1} &= \mathbf{E}_1 - \mathbf{E}_3 = 2j & Q_{C_1} &= -\frac{1}{2}\omega C_1|\mathbf{V}_{C_1}|^2 = -2 \\ \mathbf{I}_{L_1} &= \frac{\mathbf{E}_2 - \mathbf{E}_1}{j\omega L_1} = j & Q_{L_1} &= \frac{1}{2}\omega L_1|\mathbf{I}_{L_1}|^2 = \frac{1}{2} \\ Q_{tot} &= -\frac{3}{2} = \Im\{P_{c_{tot}}\} \end{aligned}$$

Soluzioni:

$$\begin{array}{lll} V_{g_1} = -2; & I_{g_1} = -1; & P c_{V_{g_1}} = 1 \\ V_{C_1} = 2j; & I_{C_1} = 2; & Q_{C_1} = -2 \\ V_{g_2} = -1 + 2j; & I_{g_2} = -1; & P c_{I_{g_2}} = \frac{1}{2} - j \\ V_{R_1} = 2 + 2j; & I_{R_1} = -1 - j; & P a_{R_1} = 2 \\ V_{R_2} = V_{L_1} = -1; & I_{R_2} + I_{L_1} = 1 - j; & P a_{R_2} = \frac{1}{2} \\ Q_{L_1} = \frac{1}{2} \\ V_{g_3} = 1 + 2j; & I_{g_3} = j; & P c_{V_{g_3}} = 1 - \frac{1}{2}j \end{array}$$