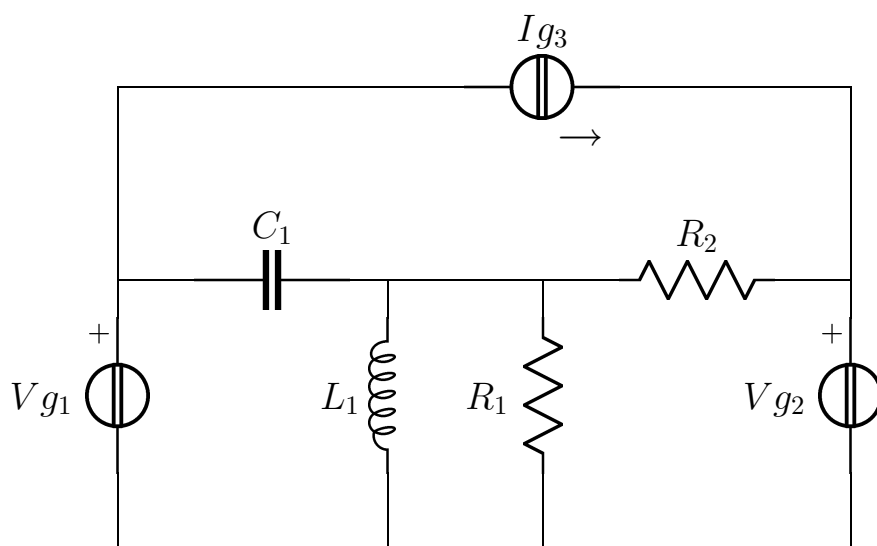


Esercizio ggcesame₂₀₁₅₋₀₂₋₁₀_{B1}*Nodirif4*

Risolvere il circuito in figura



$$\begin{aligned} \mathbf{V}_{\mathbf{g}_1} &= 2 \\ R_1 &= 1 \\ L_1 &= \frac{1}{2} \\ \mathbf{V}_{\mathbf{g}_2} &= 3 - 4j \\ C_1 &= \frac{1}{2} \\ R_2 &= 2 \\ \mathbf{I}_{\mathbf{g}_3} &= 1 - j \\ \omega &= 2 \end{aligned}$$

Semplificazioni serie/parallelo

$$Y_a = \frac{1}{R_1} + \frac{1}{j\omega L_1} = 1 - j$$

$$Z_a = \frac{1}{2} + \frac{1}{2}j$$

Risoluzione dell'esercizio con il metodo dei nodi

Sistema

$$\left\{ \begin{array}{llll} j\omega C_1 \mathbf{E}_1 & -j\omega C_1 \mathbf{E}_2 & & = -\mathbf{I}_{\mathbf{g}_3} + \mathbf{I}_{\mathbf{x}_1} \\ -j\omega C_1 \mathbf{E}_1 & +(Y_a + j\omega C_1 + \frac{1}{R_2})\mathbf{E}_2 & -\frac{1}{R_2}\mathbf{E}_3 & = 0 \\ & -\frac{1}{R_2}\mathbf{E}_2 & +\frac{1}{R_2}\mathbf{E}_3 & = \mathbf{I}_{\mathbf{g}_3} + \mathbf{I}_{\mathbf{x}_2} \\ \mathbf{E}_1 & & & = \mathbf{V}_{\mathbf{g}_1} \\ & & \mathbf{E}_3 & = \mathbf{V}_{\mathbf{g}_2} \end{array} \right.$$

Sostituzione

$$\left\{ \begin{array}{llll} j\mathbf{E}_1 & -j\mathbf{E}_2 & & = -1 + j + \mathbf{I}_{\mathbf{x}_1} \\ -j\mathbf{E}_1 & +\frac{3}{2}\mathbf{E}_2 & -\frac{1}{2}\mathbf{E}_3 & = 0 \\ & -\frac{1}{2}\mathbf{E}_2 & +\frac{1}{2}\mathbf{E}_3 & = 1 - j + \mathbf{I}_{\mathbf{x}_2} \\ \mathbf{E}_1 & & & = 2 \\ & & \mathbf{E}_3 & = 3 - 4j \end{array} \right.$$

Soluzione

$$\begin{cases} \mathbf{E}_1 = 2 \\ \mathbf{E}_2 = 1 \\ \mathbf{E}_3 = 3 - 4j \\ \mathbf{I}_{\mathbf{x}_1} = 1 \\ \mathbf{I}_{\mathbf{x}_2} = -j \end{cases}$$

Bilancio di potenza

Potenza complessa erogata dai generatori:

$$\begin{aligned} \mathbf{I}_{\mathbf{V}_{g1}} = \mathbf{I}_{\mathbf{x}_g2} = 1 & \quad P_{c_{V_{g1}}} = \frac{1}{2} \mathbf{V}_{g1} \mathbf{I}_{\mathbf{V}_{g1}}^* = 1 \\ \mathbf{I}_{\mathbf{V}_{g2}} = \mathbf{I}_{\mathbf{x}_g2} = -j & \quad P_{c_{V_{g2}}} = \frac{1}{2} \mathbf{V}_{g2} \mathbf{I}_{\mathbf{V}_{g2}}^* = 2 + \frac{3}{2}j \\ \mathbf{V}_{\mathbf{I}_{g3}} = \mathbf{E}_3 - \mathbf{E}_1 = 1 - 4j & \quad P_{c_{I_{g3}}} = \frac{1}{2} \mathbf{V}_{\mathbf{I}_{g3}} \mathbf{I}_{\mathbf{I}_{g3}}^* = \frac{5}{2} - \frac{3}{2}j \end{aligned}$$

$$P_{c_{tot}} = \frac{11}{2}$$

Potenza attiva assorbita dai resistori:

$$\begin{aligned} \mathbf{I}_{\mathbf{R}_1} = \frac{\mathbf{E}_2}{R_1} = 1 & \quad P_{a_{R_1}} = \frac{1}{2} R_1 |\mathbf{I}_{\mathbf{R}_1}|^2 = \frac{1}{2} \\ \mathbf{I}_{\mathbf{R}_2} = \frac{\mathbf{E}_3 - \mathbf{E}_2}{R_2} = 1 - 2j & \quad P_{a_{R_2}} = \frac{1}{2} R_2 |\mathbf{I}_{\mathbf{R}_2}|^2 = 5 \end{aligned}$$

$$P_{a_{tot}} = \frac{11}{2} = \Re\{P_{c_{tot}}\}$$

Potenza reattiva assorbita dai condensatori e induttori:

$$\begin{aligned} \mathbf{V}_{\mathbf{C}_1} = \mathbf{E}_2 - \mathbf{E}_1 = -1 & \quad Q_{C_1} = -\frac{1}{2} \omega C_1 |\mathbf{V}_{\mathbf{C}_1}|^2 = -\frac{1}{2} \\ \mathbf{I}_{\mathbf{L}_1} = \frac{\mathbf{E}_2}{j\omega L_1} = -j & \quad Q_{L_1} = \frac{1}{2} \omega L_1 |\mathbf{I}_{\mathbf{L}_1}|^2 = \frac{1}{2} \end{aligned}$$

$$Q_{tot} = 0 = \Im\{P_{c_{tot}}\}$$

Soluzioni:

$$\begin{aligned} V_{g1} = 2; \quad I_{g1} = 1; \quad P_{c_{V_{g1}}} = 1 \\ V_{R1} = V_{L1} = 1; \quad I_{R1} + I_{L1} = -1 + j; \quad P_{a_{R1}} = \frac{1}{2} \\ Q_{L1} = \frac{1}{2} \\ V_{g2} = 3 - 4j; \quad I_{g2} = -j; \quad P_{c_{V_{g2}}} = 2 + \frac{3}{2}j \\ V_{C1} = -1; \quad I_{C1} = j; \quad Q_{C1} = -\frac{1}{2} \\ V_{R2} = 2 - 4j; \quad I_{R2} = -1 + 2j; \quad P_{a_{R2}} = 5 \\ V_{g3} = 1 - 4j; \quad I_{g3} = 1 - j; \quad P_{c_{I_{g3}}} = \frac{5}{2} - \frac{3}{2}j \end{aligned}$$